



100-1 Under-Graduate Project

Verilog

Speaker: 洪輝舜

Adviser: Prof. An-Yeu Wu

Date: 2011/9/27



Outline

- ❖ Basic Concept of Verilog HDL
- ❖ Gate Level Modeling
- ❖ Simulation & Verification
- ❖ Summary




What is Verilog HDL ?

- ❖ Hardware Description Language
- ❖ Mixed level modeling
 - ❖ Behavioral
 - Algorithmic (like high level language)
 - Register transfer (Synthesizable)
 - ❖ Register Transfer Level (RTL)
 - Describing a system by the flow of data and control signals within and between functional blocks
 - Define the model in terms of cycles, based on a defined clock
 - ❖ Structural
 - Gate (AND, OR)
 - Switch (PMOS, NOMS, JFET)



An Example

1-bit Multiplexer

 


```
if (sel==0)
    out=in1;
else
    out=in2;
```

| sel | in1 | in2 | out |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

$$\text{out} = (\text{sel}' \text{ in1}) + (\text{sel in2})$$



Gate Level Description

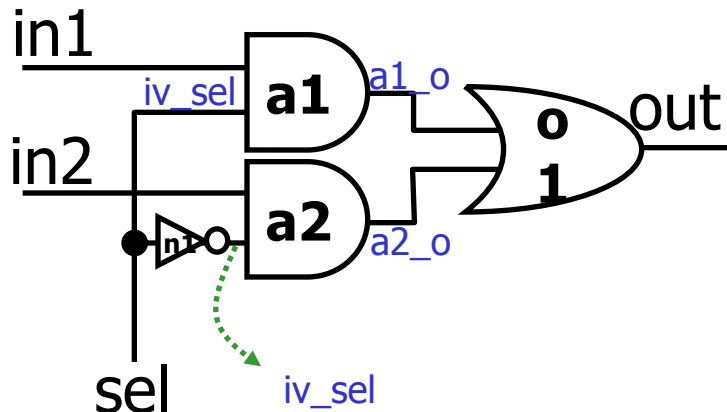

```
module mux2(out,in1,in2,sel);  
    output    out;  
    input     in1,in2,sel;  
  
    and a1(a1_o,in1,sel);  
    not n1(iv_sel,sel);  
    and a2(a2_o,in2,iv_sel);  
    or  o1(out,a1_o,a2_o);  
endmodule
```

Gate Level: you see only netlist (gates and wires) in the code



Verilog Language Rules


- ❖ Verilog is a **case sensitive** language (with a few exceptions)
- ❖ Identifiers (space-free sequence of symbols)
 - ❖ upper and lower case letters from the alphabet
 - ❖ digits (0, 1, ..., 9) (cannot be the first character)
 - ❖ underscore (_)
 - ❖ \$ symbol (only for system tasks and functions)
 - ❖ Max length of 1024 symbols
- ❖ Terminate lines with semicolon ;
- ❖ Single line comments:
 - ❖ // A single-line comment goes here
- ❖ Multi-line comments:
 - ❖ /* Multi-line comments like this */

```
/* Verilog HDL module
   Half adder
*/
module adder (out0,in1,in2);
    output [1:0] out0;
    input      in1,in2;

    assign out0 = in1 + in2
endmodule //end of module
```



Verilog HDL Syntax

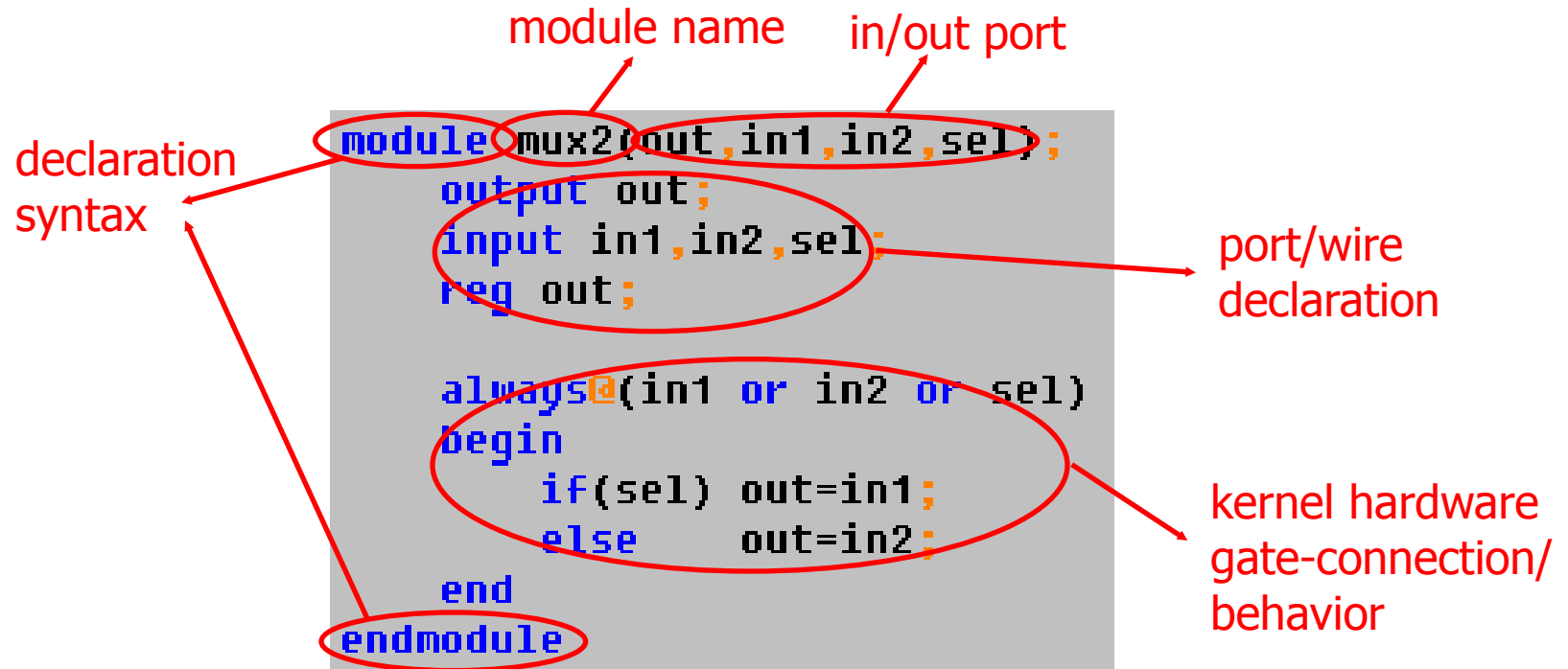



Module

- ❖ Basic building block in Verilog.
- ❖ Module
 1. Created by “declaration” (**can't be nested**)
 2. Used by “instantiation”
- ⊕ Interface is defined by ports
- ⊕ May contain instances of other modules
- ⊕ All modules run concurrently



Instances

- ❖ A module provides a template from which you can create actual objects.
- ❖ When a module is invoked, Verilog creates a unique object from the template.
- ❖ Each object has its own name, variables, parameters and I/O interface.




Module Instantiation

```
module adder(out,in1,in2);  
    output out;  
    input in1,in2,sel;  
  
    assign out=in1 + in2;  
endmodule
```

instance
example
 
```
module adder_tree (out0,out1,in1,in2,in3,in4);  
    output out0,out1;  
    input in1,in2,in3,in4;  
  
    adder add_0 (out0,in1,in2);  
    adder add_1 (out1,in3,in4);  
endmodule
```





Port Connection

```
module FA1 (CO,S,A,B,CI);  
    output CO,S;  
    input A,B,CI;  
  
    assign {CO,S} = A+B+CI;  
endmodule
```


- ❖ Connect module port by order list
 - FA1 fa1(c_o, sum, a, b, c_i);
- ❖ Connect module port by name *.PortName(NetName)*
 - FA1 fa2(.A(a), .B(b), .CO(c_o),.CI(c_i), .S(sum));
 - Recommended



Value Sets

❖ 4-value logic system in Verilog

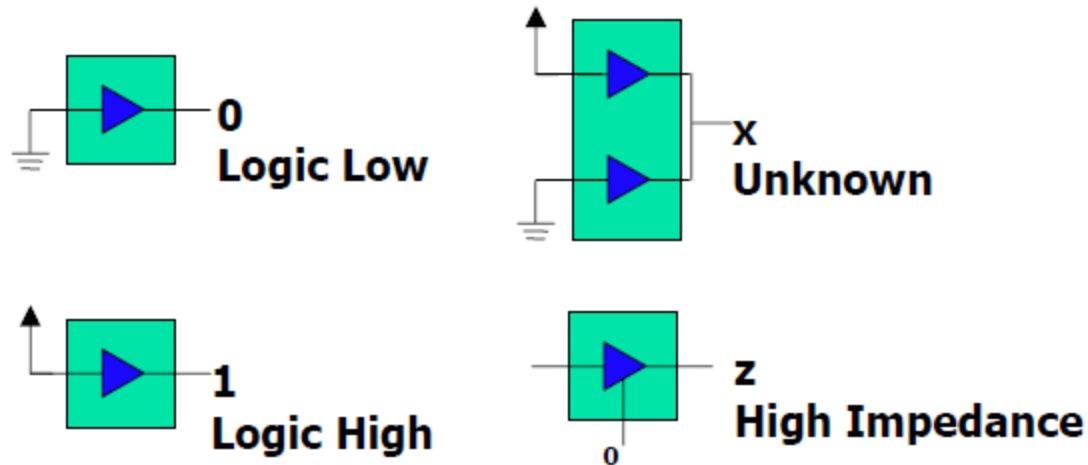❖ Four values: 0, 1, x or X, z or Z // Not case sensitive here





Register and Net

❖ Registers

- ❖ Keyword : **reg**, integer, time, real
- ❖ Event-driven modeling
- ❖ Storage element (modeling sequential circuit)
- ❖ Assignment in “always” block
- ❖ Default value is X

❖ Nets

- ❖ Keyword : **wire**, wand, wor, tri
triand, trior, supply0, supply1
- ❖ Doesn't store value, just a connection
- ❖ input, output, inout are default “wire”
- ❖ Can't appear in “always” block assignment
- ❖ Default value is Z



Wire & Reg


- ❖ reg
 - ❖ A variable in Verilog
- ❖ Use of “reg” data type is not exactly synthesized to a really register.
- ❖ Use of wire & reg
 - ❖ When use “wire” → usually use “assign” and “assign” **does not** appear in “always” block
 - ❖ When use “reg” → only use “a=b” , always appear in “always” block

```
module test(a,b,c,d);  
input a,b;  
output c,d;  
reg d;  
assign c=a;  
always @(b)  
    d=b;  
endmodule
```



Choosing the Correct Data Types

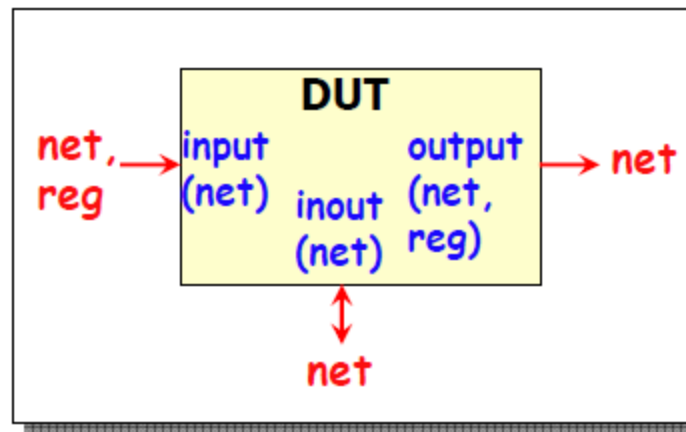- ❖ An **input** or **inout** port must be a **net**.
- ❖ An **output** port can be a **register data type**.
- ❖ A signal assigned a value in a procedural block must be a **register data type**.





Number Representation

❖ Format: <size>'<base_format><number>

❖ <size> - decimal specification of number of bits

➤ default is unsized and machine-dependent but at least 32 bits

❖ <base format> - ' followed by arithmetic base of number

➤ <d> <D> - decimal - default base if no <base_format> given

➤ <h> <H> - hexadecimal

➤ <o> <O> - octal

➤ - binary

❖ <number> - value given in base of <base_format>

➤ _ can be used for reading clarity

➤ If first character of sized, binary number 0, 1, x or z, will extend 0, 1, x or z (defined later!)



Number Representation

❖ Examples:

- ❖ 6'b010_111 gives 010111
- ❖ 8'b0110 gives 00000110
- ❖ 4'bx01 gives xx01
- ❖ 16'H3AB gives 0000001110101011
- ❖ 24 gives 0...0011000
- ❖ 5'O36 gives 11110
- ❖ 16'Hx gives xxxxxxxxxxxxxxxxx
- ❖ 8'hz gives zzzzzzzz



Net Concatenations

❖ A easy way to group nets

| Representation | Meanings |
|---------------------|--|
| {cout, sum} | {cout, sum} |
| {b[7:4],c[3:0]} | {b[7], b[6], b[5], b[4], c[3], c[2], c[1], c[0]} |
| {a,b[3:1],c,2'b10} | {a, b[3], b[2], b[1], c, 1'b1, 1'b0} |
| {4{2'b01}} | 8'b01010101 |
| {{8{byte[7]}},byte} | Sign extension |



Compiler Directives

❖ *`define*

- ❖ *`define* RAM_SIZE 16

- ❖ Defining a name and gives a constant value to it.

❖ *`include*

- ❖ *`include* adder.v

- ❖ Including the entire contents of other verilog source file.

❖ *`timescale*

- ❖ *`timescale* 100ns/1ns

- ❖ Setting the reference time unit and time precision of your simulation.



System Tasks

❖ *\$monitor*

- ❖ *\$monitor (\$time, "%d %d %d", address, sinout, cosout);*
- ❖ Displays the values of the argument list whenever any of the arguments change except \$time.

❖ *\$display*

- ❖ *\$display ("%d %d %d", address, sinout, cosout);*
- ❖ Prints out the current values of the signals in the argument list

❖ *\$finish*

- ❖ *\$finish*
- ❖ Terminate the simulation



Gate Level Modeling



Gate Level Modeling

❖ Steps

- ❖ Develop the boolean function of output
- ❖ Draw the circuit with logic gates/primitives
- ❖ Connect gates/primitives with net (usually wire)
- ❖ HDL: Hardware **Description** Language
 - ❖ Figure out architecture first, then write code.




Primitives

- ❖ Primitives are modules ready to be instanced
- ❖ Smallest modeling block for simulator
- ❖ Verilog build-in primitive gate
 - ❖ *and, or, not, buf, xor, nand, nor, xnor*
 - ❖ `prim_name inst_name(output, in0, in1,....);`
 - EX. `and g0(a, b, c);`
- ❖ User defined primitive (UDP)
 - ❖ building block defined by designer



Case Study

1-bit Full Adder

 


| Ci | A | B | Co | S |
|----|---|---|----|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |



Case Study

1-bit Full Adder

 ❖ $co = (a \cdot b) + (b \cdot ci) + (ci \cdot a);$






```
30
31 module FA_co ( co, a, b, ci );
32
33     input    a, b, ci;
34     output   co;
35     wire     ab, bc, ca;
36
37     and g0( ab, a, b );
38     and g1( bc, b, c );
39     and g2( ca, c, a );
40     or  g3( co, ab, bc, ca );
41
42 endmodule
43
```



Case Study

1-bit Full Adder
   
$$\diamond \text{sum} = a \oplus b \oplus ci$$



```
44 module FA_sum ( sum, a, b, ci );  
45  
46     input    a, b, ci;  
47     output   sum, co;  
48  
49     xor g1( sum, a, b, ci );  
50  
51 endmodule  
52
```



Case Study


1-bit Full Adder

❖ Full Adder Connection

❖ Instance *ins_c* from FA_co

❖ Instance *ins_s* from FA_sum
 
```
20
21 module FA_gatelevel( sum, co, a, b, ci );
22
23     input    a, b, ci;
24     output   sum, co;
25
26     FA_co    ins_c( co, a, b, ci );
27     FA_sum    ins_s( sum, a, b, ci );
28
29 endmodule
30
```






Timing and Delays



Delay Specification in Primitives

- ❖ Delay specification defines the propagation delay of that primitive gate.

not #10 (out,in);

 




Types of Delay Models

❖ Distributed Delay

 - ❖ Specified on a per element basic
- ❖ Delay value are assigned to individual in the circuit




```
module and4(out, a, b, c, d);
    ... ..
    and #5 a1(e, a, b);
    and #7 a2(f, c, d);
    and #4 a3(out, e, f);
endmodule
```



Types of Delay Models

❖ Lumped Delay

 - ❖ They can be specified as a single delay on the output gate of the module
- ❖ The cumulative delay of all paths is lumped at one location




```
module and4(out, a, b, c, d);  
    ... ..  
    and    a1(e, a, b);  
    and    a2(f, c, d);  
    and #11 a3(out, e, f);  
endmodule
```



Types of Delay Models

❖ Pin-to-Pin Delay

 - ❖ Delays are assigned individually to paths from each input to each output.
- ❖ Delays can be separately specified for each input/output path.



Path a-e-out, delay = 9

Path b-e-out, delay = 9


Path c-f-out, delay = 11

Path d-f-out, delay = 11



Timing Checks

❖ setup and hold checks

 

```
specify  
  $setup(data, posedge clock, 3);  
endspecify
```

```
specify  
  $hold(posedge clock, data, 5);  
endspecify
```




Simulation & Verification



Test Methodology

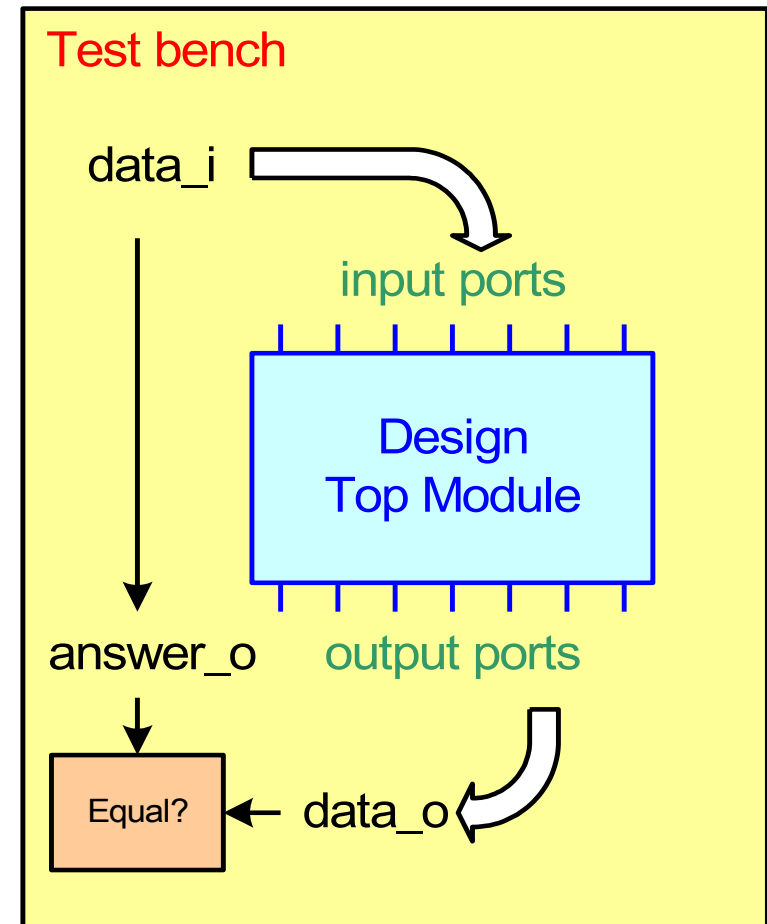- ❖ Systematically verify the functionality of a model.
- ❖ Simulation:
 - (1) detect syntax violations in source code
 - (2) simulate behavior
 - (3) monitor results






Testbench for Full Adder

```
module t_full_add();  
    reg    a, b, cin;           // for stimulus waveforms  
    wire   sum, c_out;  
  
    full_add M1 (sum, c_out, a, b, cin); //DUT  
  
    initial #200 $finish;       // Stopwatch  
  
    initial begin               // Stimulus patterns  
        $fsdbDumpfile("t_full_add.fsdb");  
        $fsdbDumpvars;  
        #10 a = 0; b = 0; cin = 0; // Statements execute in sequence  
        #10 a = 0; b = 1; cin = 0;  
        #10 a = 1; b = 0; cin = 0;  
        #10 a = 1; b = 1; cin = 0;  
        #10 a = 0; b = 0; cin = 1;  
        #10 a = 0; b = 1; cin = 1;  
        #10 a = 1; b = 0; cin = 1;  
        #10 a = 1; b = 1; cin = 1;  
    end  
endmodule
```



Simulation Results

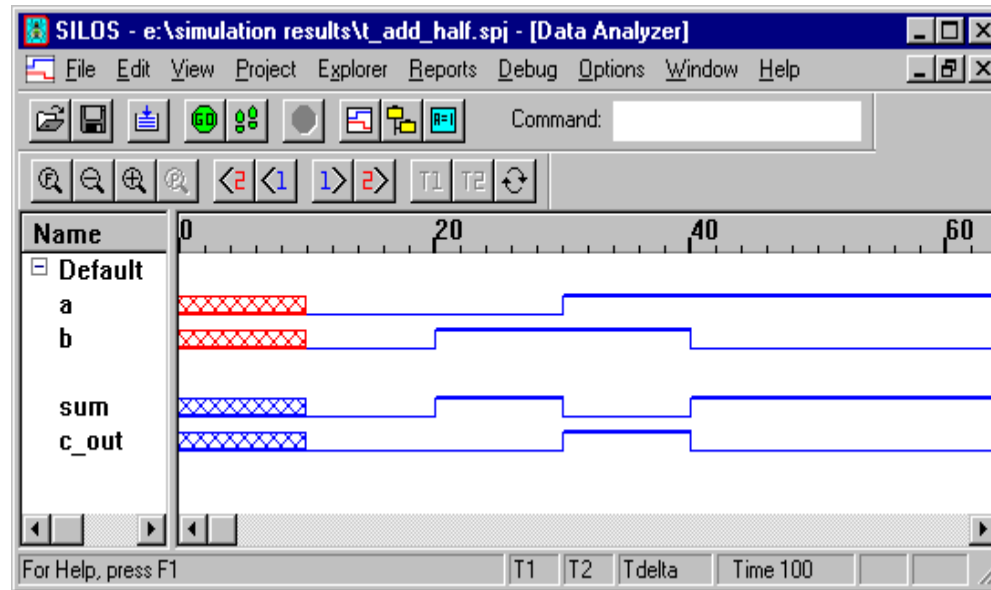

MODELING TIP

A Verilog simulator assigns an *initial* value of **x** to all variables.



Example: Propagation Delay

❖ Unit-delay simulation reveals the chain of events


```
module Add_full (sum, c_out, a, b, c_in);  
  output          sum, c_out;  
  input           a, b, c_in;  
  wire            w1, w2, w3;
```

```
  Add_half          M1 (w1, w2, a, b);  
  Add_half          M2 (sum, w3, w1, c_in);  
  or                #1      M3 (c_out, w2, w3);  
endmodule
```

```
module Add_half (sum, c_out, a, b);  
  output          sum, c_out;  
  input           a, b;  
  
  xor             #1 M1 (sum, a, b); // single delay value format  
  and             #1 M2 (c_out, a, b); // others are possible  
endmodule
```



Simulation with delay

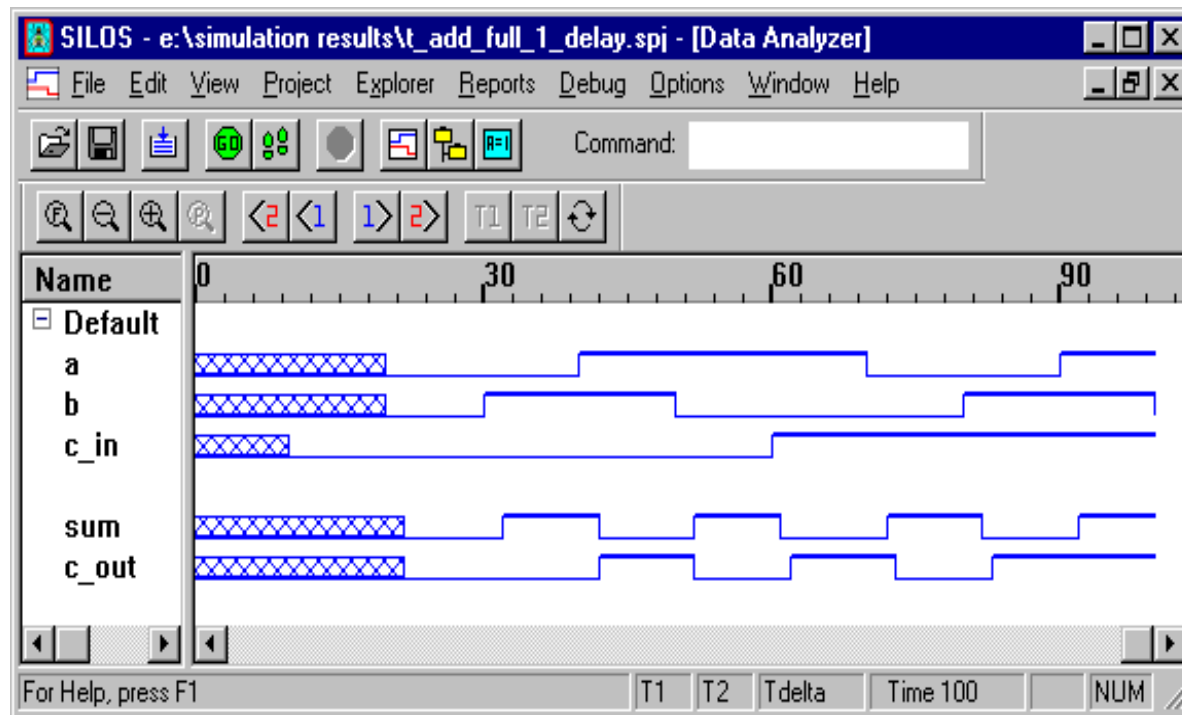



Summary

❖ Design module

- ❖ Gate-level or RT-level
- ❖ Real hardware
 - Instance of modules exist all the time
- ❖ Each module has architecture figure
 - Plot architecture figures before you write verilog codes

❖ Test bench

- ❖ Feed input data and compare output values versus time
- ❖ Usually behavior level
- ❖ Not real hardware, just like C/C++



Note

- ❖ Verilog is a platform
 - Support hardware design (design module)
 - Also support C/C++ like coding (test bench)
- ❖ How to write verilog well
 - Know basic concepts and syntax
 - Get a good reference (a person or some code files)
 - Form a good coding habit
 - Naming rule, comments, format partition (assign or always block)
- ❖ Hardware
 - Combinational circuits
 - 畫圖(architecture), then 連連看(coding)
 - Sequential circuits
 - register: element to store data