



100-1 Under-Graduate Project

Synthesis of Combinational Logic

Speaker: Kuanyu Ho

Adviser: Prof. An-Yeu Wu

Date: 2011/10/18



Outline

- ❖ What is synthesis?
- ❖ Behavior Description for Synthesis
- ❖ Write Efficient HDL Code



What is logic synthesis

- ❖ Logic synthesis is the process of converting a high-level description of design into an optimized gate-level representation
- ❖ Logic synthesis uses standard cell library which have simple cells, such as basic logic gates like **and**, **or**, and **nor**, or macro cells, such as adder, muxes, memory, and special flip-flops
- ❖ The designer would first understand the architectural description. Then he/she would consider design constraints such as timing, area, testability, and power




What is logic synthesis

❖ Synthesis = translation + optimization + mapping

```
residue = 16'h0000;  
if ( high_bits == 2'b10)  
    residue = state_table[index];  
else state_table[index] =16'h0000;
```


HDL Source

Translate

 

**Generic Boolean
(GTECH)**


Optimize + Map

 

Target Technology




Synthesis is Constraint Driven

 




Technology Independent

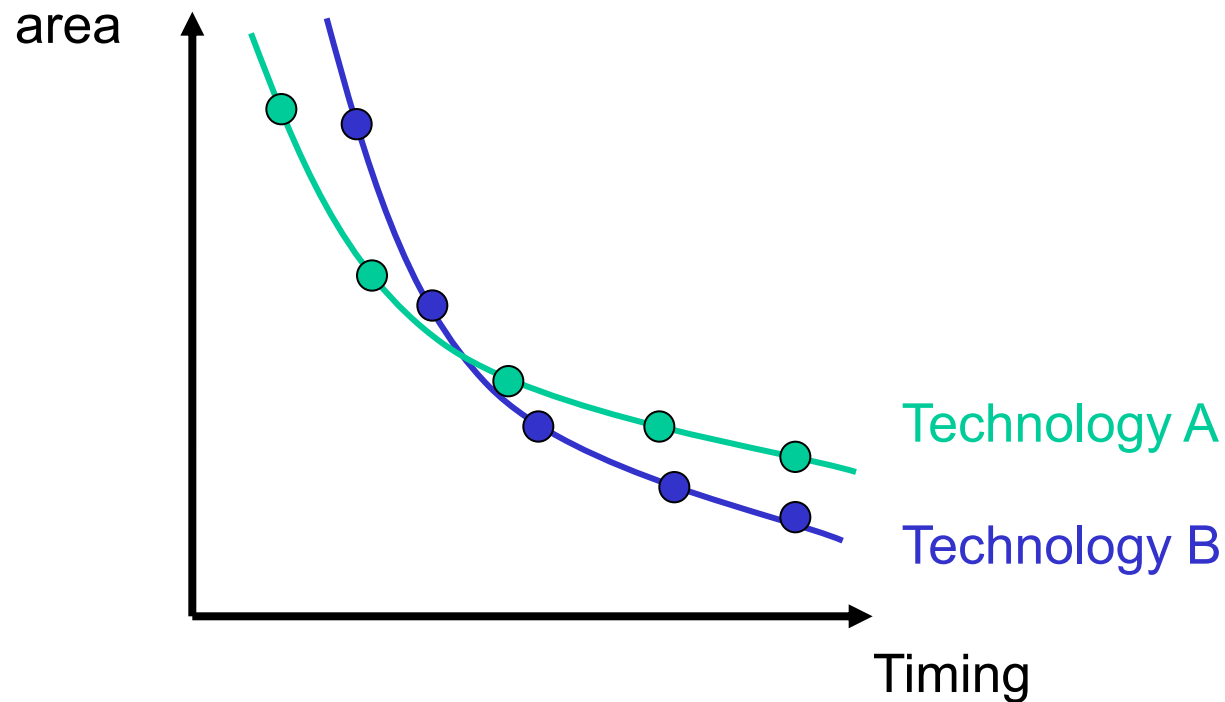- ❖ Design can be transferred to any technology





What is logic synthesis(cont.)

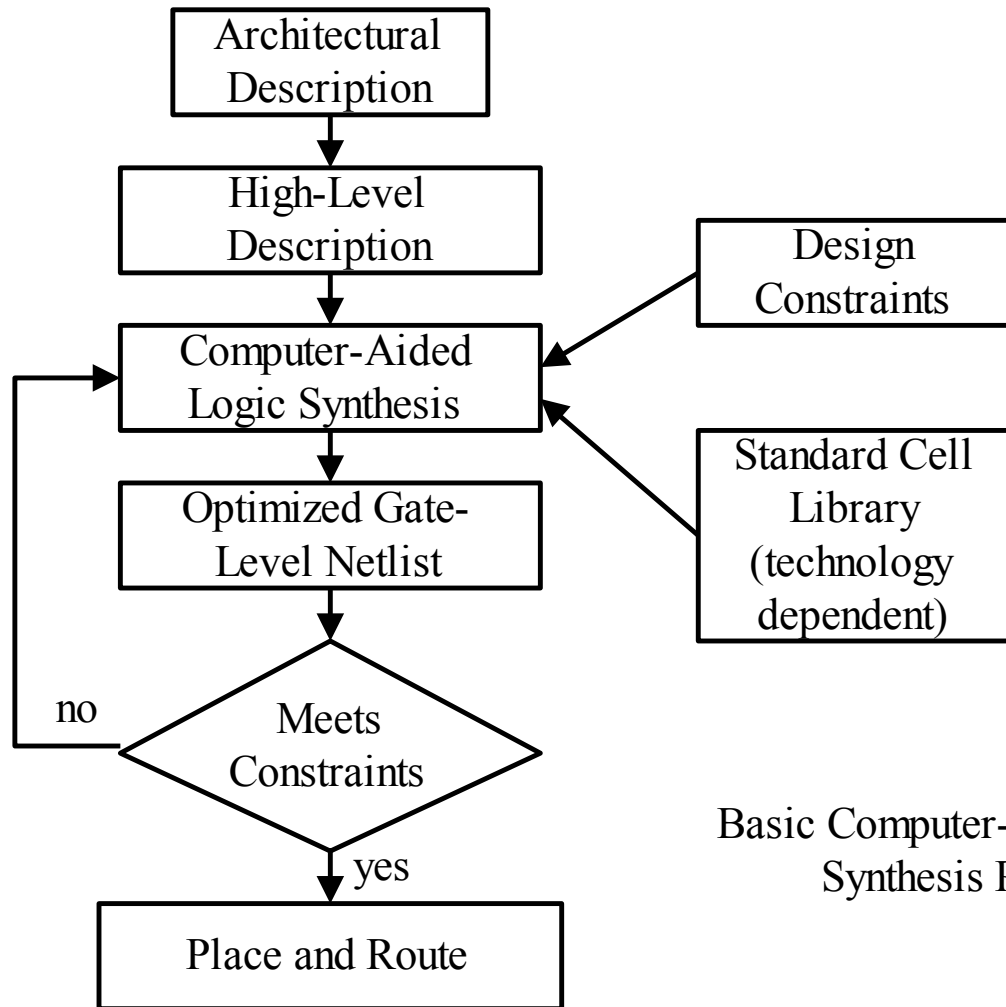

Basic Computer-Aided Logic
Synthesis Process



Impact of Logic Synthesis

❖ Limitation on manual design

- ❖ For large designs, manual conversion was prone human error, such as a small gate missed somewhere
- ❖ The designer could never be sure that the design constraints were going to be met until the gate-level implementation is complete and tested
- ❖ A significant portion of the design cycle was dominated by the time taken to convert a high-level design into gates
- ❖ Design reuse was not possible
- ❖ Each designer would implement design blocks differently. For large designs, this could mean that smaller blocks were optimized but the overall design was not optimal




Impact of Logic Synthesis(cont.)

- ❖ Automated Logic synthesis tools addressed these problems as follows
 - ❖ High-level design is less prone to human error because designs are described at a higher level of abstraction
 - ❖ High-level design is done without significant concern about design constraints
 - ❖ Conversion from high-level design to gates is fast
 - ❖ Logic synthesis tools optimize the design as a whole. This removes the problem with varied designer styles for the different blocks in the design and suboptimal designs
 - ❖ Logic synthesis tools allow technology-independent design
 - ❖ Design reuse is possible for technology-independent descriptions.



Logic Synthesis

- ❖ Takes place in two stages:

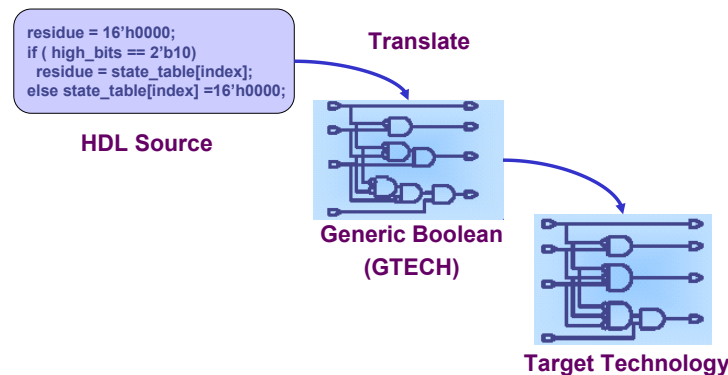

- ❖ Translation of Verilog (or VHDL) source to a netlist
 - ❖ Register inference
- ❖ Optimization of the resulting netlist to improve speed and area
 - ❖ Most critical part of the process
 - ❖ Algorithms very complicated and beyond the scope of this class



Combinational vs. Sequential Mapping

Combinational Mapping

- ❖ Mapping rearranges components, combining and re-combining logic into different components
- ❖ May use different algorithms such as cloning, resizing or buffering
- ❖ Try to meet the design rule constraints and timing/area goals


Sequential Mapping

- ❖ Optimize the mapping to sequential cells from technology library
- ❖ Analyze combinational surrounding a sequential cell to see if it can absorb the logic attribute with HDL
- ❖ Try to save speed and area by using a more complex sequential cell




Mapping

Combinational mapping

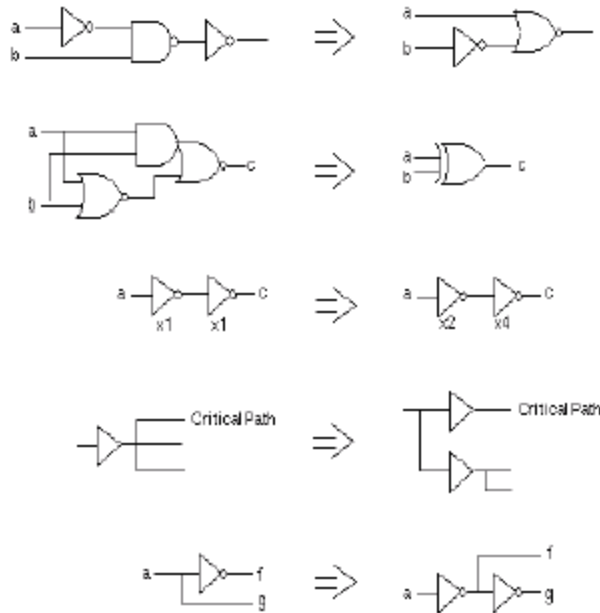


Sequential mapping

 



Design Methodology

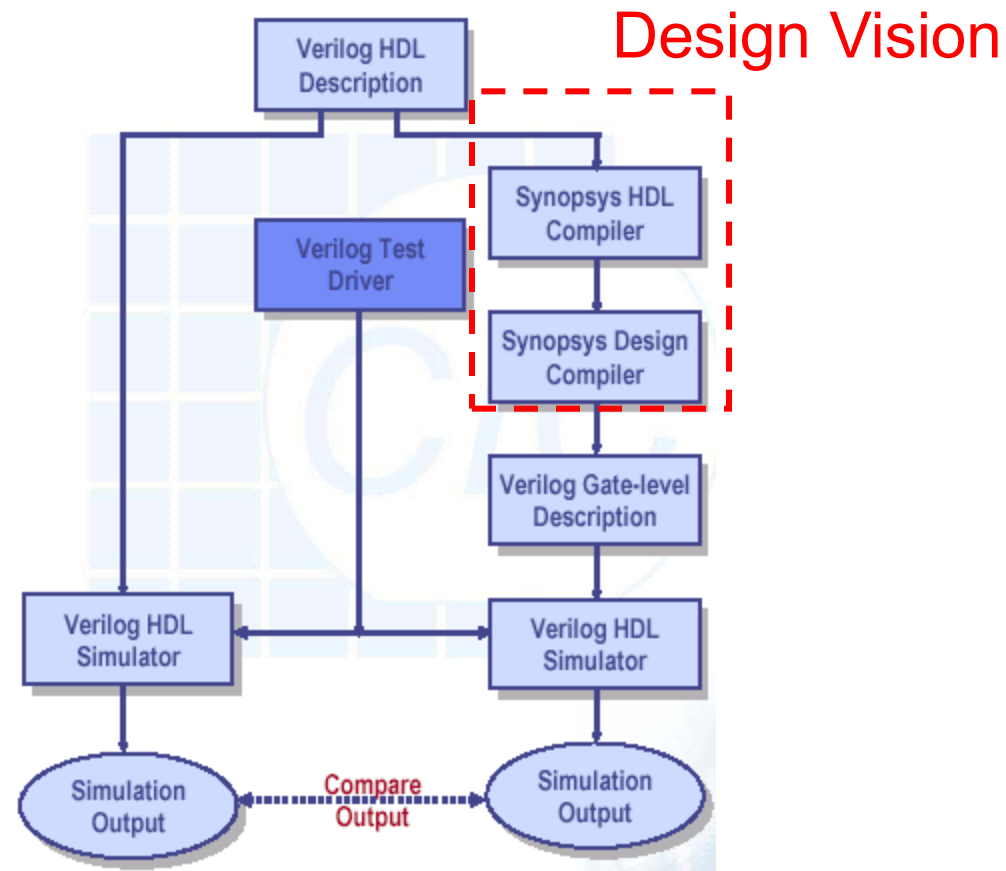



Verilog and Logic Synthesis

- ❖ Verilog is used in two ways
 - ❖ Model for discrete-event simulation
 - ❖ Specification for a logic synthesis system
- ❖ Logic synthesis converts a subset of the Verilog language into an efficient netlist
- ❖ One of the major breakthroughs in designing logic chips in the last 20 years
- ❖ Most chips are designed using at least some logic synthesis



Verilog Primitive Cell

- ❖ Verilog primitive cells build basic combinational circuit
- ❖ Synthesizable Verilog primitives cells
 - ❖ and, nand, or, nor, xor, xnor, not
 - ❖ bufif0, bufif1, notif0, notif1



What Isn't Translated

❖ Initial blocks

- ❖ Used to set up initial state or describe finite testbench stimuli
- ❖ Don't have obvious hardware component

❖ Delays

- ❖ May be in the Verilog source, but are simply ignored

❖ A variety of other obscure language features

- ❖ In general, things heavily dependent on discrete-event simulation semantics
- ❖ Certain "disable" statements
- ❖ Pure events



HDL Compiler Unsupported

- ❖ delay
- ❖ initial
- ❖ repeat
- ❖ wait
- ❖ fork ... join
- ❖ event
- ❖ deassign
- ❖ force
- ❖ release
- ❖ primitive -- User defined primitive (Sequential)
- ❖ time
- ❖ triand, trior, tri1, tri0, trireg
- ❖ nmos, pmos, cmos, rnmos, rpmos, rcmos
- ❖ pullup, pulldown
- ❖ rtran, tranif0, tranif1, rtranif0, rtranif1
- ❖ case identity and not identity operators
- ❖ Division and modulus operators
 - ❖ division can be done using DesignWare instantiation



Verilog Operators Supported

- ❖ Binary bit-wise ($\sim, \&, |, ^, \sim^{\wedge}$)
- ❖ Unary reduction ($\&, \sim\&, |, \sim|, ^, \sim^{\wedge}$)
- ❖ Logical ($!, \&\&, ||$)
- ❖ 2's complement arithmetic ($+, -, *, /, \%$)
- ❖ Relational ($>, <, >=, <=$)
- ❖ Equality ($==, !=$)
- ❖ Logical shift ($>>, <<$)
- ❖ Conditional ($?:$)



always Block

❖ Example

```
always @(event-expression )  
begin  
    statements  
end
```

- ❖ If event-expression contains **posedge** or **negedge**, **flip-flop** will be synthesized.
- ❖ In all other cases, **combinational** logic will be synthesized.
- ❖ A variable assigned within an always @ block that is not fully specified will result in **latches** synthesized.



Latch Inference


- ❖ A variable assigned within an always block that is not fully specified.
- ❖ If a case statement is not a full case, it will infer a latch.



Register Inference

- ❖ A register (flip-flop) is implied when you use the `@(posedge clk)` or `@(negedge clk)` in an always block.
- ❖ Any variable that is assigned a value in this always block is synthesized as a **D-type** edge-triggered flip-flop.
 
```
always @(posedge clk)
  out <= a & b;
```






Combinational Logic Inference

- ❖ Not all variables declared as **reg** data type need a flip-flop or a latch for logic implementation.
 
```
reg data_out;  
always @(a or b or c)  
if (b)  
    data_out = a;  
else  
    data_out = c;
```





Comparisons to X or Z

- ❖ Comparisons to an X or Z are always ignored.
- ❖ Comparison is always evaluated to false, which may cause simulation & synthesis mismatch.

```
module  
compare_x(A,B);  
input A;  
output B;  
reg B;  
always begin  
if (A== 1'bx)  
    B=0;  
else  
    B=1;  
end  
endmodule
```


Warning: Comparisons to a “don't care” are treated as always being false in routine compare_x line 7 in file “compare_x.v” this may cause simulation to disagree with synthesis. (HDL-170)

Always
false



Non-Blocking and Blocking

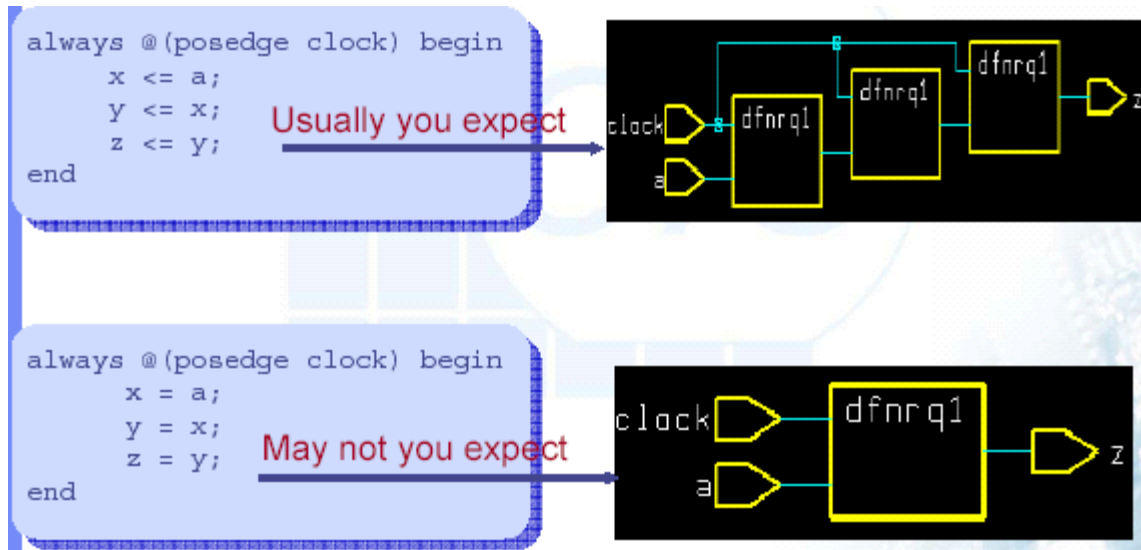- ❖ For the most straightforward code:
(you get what you expect)
 - ❖ Use **non-blocking** assignments within sequential always block.
 - ❖ Example:






Non-Blocking and Blocking

- ❖ For the most straightforward code:
(you get what you expect)
 - ❖ Use **blocking** assignments within combinational always block.
 - ❖ Example:


```
always @(a or b or x) begin
    x = a & b;
    y = x | b;
    x = a;
end
```

Usually you expect

 

```
always @(a or b or x) begin
    x <= a & b;
    y <= x | b;
    x <= a;
end
```

May not you expect

 




Resource Sharing

- ❖ Operations can be shared if they lie in the same always block.
 
```
always @(a or b or c or sel)
  if (sel)
    z=a+b;
  else
    z=a+c;
```






Combinational Always Block

- ❖ Sensitivity list must be specified completely, otherwise synthesis may mismatch with simulation

```
always @(a or b or c)  
f=a&b|c;
```

```
always @(a or b)  
f=a&b|c;
```

 

Warning: Variable 'c' is being read
in routine train line 6 in file '/ccyang/abc/train1.v',
but does not occur in the timing control of the block which begins
there. (HDL-180)



if Statement

- ❖ Provide for more complex conditional actions, each condition expression controls a multiplexer legal only in function & always construct
- ❖ Syntax


```
if (expr )  
begin  
... statements ...  
end  
else  
begin  
... statements ...  
end
```



if Statement

❖ if statement can be nested
 
```
always @(sel1 or sel2 or sel3 or sel4 or in1  
or in2 or in3 or in4 or in5)  
begin  
  if (sel1) begin  
    if (sel2) out=in1;  
    else out=in2;  
  end  
  else if (sel3) begin  
    if (sel4) out=in3;  
    else out=in4;  
  end  
  else out=in5;  
end
```





if Statement

❖ What's the difference between these two coding styles?

```
module mult_if(a, b, c, d, e, sel, z);  
input a, b, c, d, e;  
input [3:0] sel;  
output z;  
reg z;  
always @(a or b or c or d or e or sel)  
begin  
    z = e;  
    if (sel[0]) z = a;  
    if (sel[1]) z = b;  
    if (sel[2]) z = c;  
    if (sel[3]) z = d;  
end  
endmodule
```

```
module single_if(a, b, c, d, e, sel, z);  
input a, b, c, d, e;  
input [3:0] sel;  
output z;  
reg z;  
always @(a or b or c or d or e or sel)  
begin  
    z = e;  
    if (sel[3])  
        z = d;  
    else if (sel[2])  
        z = c;  
    else if (sel[1])  
        z = b;  
    else if (sel[0])  
        z = a;  
    end  
end  
endmodule
```

Priority of sel[3] is highest



case Statement

- ❖ Legal only in the function & always construct
- ❖ syntax


```
case ( expr )  
    case_item1: begin  
        ... statements ...  
    end  
    case_item2: begin  
        ... statements ...  
    end  
    default: begin  
        ... statements ...  
    end  
endcase
```



case Statement

- ❖ A case statement is called a **full case** if all possible branches are specified.
 
```
always @(bcd) begin
  case (bcd)
    4'd0:out=3'b001;
    4'd1:out=3'b010;
    4'd2:out=3'b100;
    default:out=3'b000;
  endcase
end
```






case Statement

- ❖ If a case statement is **not** a full case, it will infer a **latch**.
 
```
always @(bcd) begin
  case (bcd)
    4'd0:out=3'b001;
    4'd1:out=3'b010;
    4'd2:out=3'b100;
  endcase
end
```





case Statement

❖ **Note:** the second case item does not modify reg2, causing it to be inferred as a latch (to retain last value).

```
case (cntr_sig) // synopsys full_case
  2'b00 : begin
    reg1 = 0 ;
    reg2 = v_field ;
  end
  2'b01 : reg1 = v_field ; /* latch will be inferred for reg2*/

  2'b10 : begin
    reg1 = v_field ;
    reg2 = 0 ;
  end
endcase
```

reg1 -> combinational
reg2 -> latch



case Statement

- ❖ Two possible ways we can assign a default value to next_state.

```
(1)  out = 3'b000 ; // this is called unconditional assignment
      case (condition)
      ...
      endcase
```


```
(2)  case (condition)
      ...
      default : out = 3'b000 ; // out=0 for all other cases
      endcase
```



case Statement

- ❖ If HDL Compiler can't determine that case branches are parallel, its synthesized hardware will include a priority decoder.
 
```
always @(u or v or w or x or y or z)
begin
  case (2'b11)
    u:out=10'b0000000001;
    v:out=10'b0000000010;
    w:out=10'b0000000100;
    x:out=10'b0000001000;
    y:out=10'b0000010000;
    z:out=10'b0000100000;
    default:out=10'b0000000000;
  endcase
end
```






case Statement

- ❖ If you can be sure that only one variable will be "11" at one time.
- ❖ You can declare a case statement as parallel case with the `//synopsys parallel_case` directive.
 
```
always @(u or v or w or x or y or z)
begin
  case (2'b11) //synopsys parallel_case
    u:out=10'b0000000001;
    v:out=10'b0000000010;
    w:out=10'b0000000100;
    x:out=10'b0000001000;
    y:out=10'b0000010000;
    z:out=10'b0000100000;
    default:out=10'b0000000000;
  endcase
end
```





if vs. case

❖ Recommendations:

- ❖ If the “if else” chain is **too long**, use “case” statement to replace them.
- ❖ If you can know the conditions of “case” statement are **mutually exclusive**, please use synopsys directive “`//synopsys parallel_case`” in order to let design compiler to create a **parallel decoder** for you.
- ❖ If you know the conditions of a “case” statement, which is not listed, will never occur, please use “`//synopsys full_case`” directive in order to prevent latches been synthesized.



for Loop

- ❖ Provide a shorthand way of writing a series of statements.
- ❖ Loop index variables must be integer type.
- ❖ Step, start & end value must be constant.
- ❖ In synthesis, for loops are “unrolled”, and then synthesized.
- ❖ Example

```
always @(a or b) begin
    for( k=0; k<=3; k=k+1 ) begin
        out[k]=a[k]^b[k];
        c=(a[k] | b[k])&c;
    end
end
```

```
out[0] = a[0]^b[0];
out[1] = a[1]^b[1];
out[2] = a[2]^b[2];
out[3] = a[3]^b[3];
c = (a[0] | b[0]) & (a[1] | b[1]) &
    a[2] | b[2]) & (a[3] | b[3]) & c;
```




Write Efficient HDL Code

- ❖ Use parentheses control complex structure of a design.
- ❖ Use operator bit-width efficiently.
- ❖ Data-path Duplication
- ❖ Operator in “if” statement



Use Parentheses Properly


❖ $\text{Out} = a + b + c + d + e + f;$

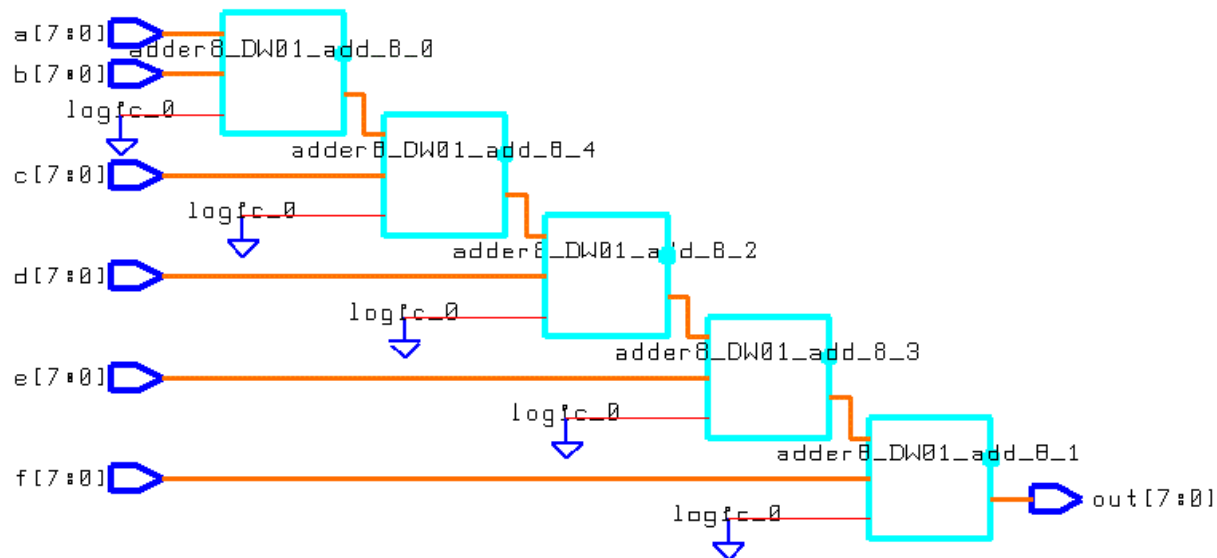



Use Parentheses Properly(cont.)

❖ $\text{Out} = (a+b) + (c+d) + (e+f);$

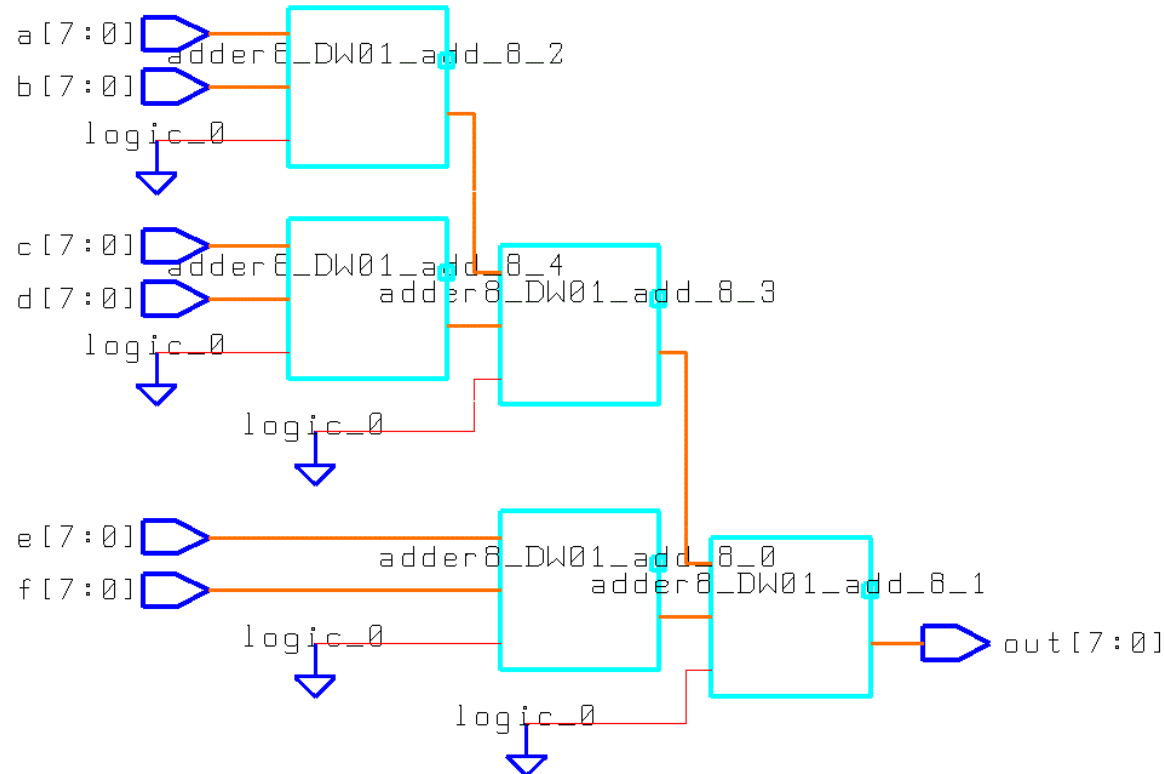



Use Operator Bit-Width Efficiently

```
module test(a,b,out);  
  input [7:0] a,b;  
  output [8:0] out;  
  assign out=add_lt_10(a,b);  
  
  function [8:0] add_lt_10;  
    input [7:0] a,b;  
    reg [7:0] temp;  
    begin  
      if (b<10) temp=b;  
      else temp=10;  
      add_lt_10=a+temp[3:0]; //use [3:0] for temp  
    end  
  endfunction  
  
endmodule
```

HHHHFFFFH



Coding Skill-Data-path Duplication

No_duplicated

```
module BEFORE (ADDRESS, PTR1, PTR2, B, CONTROL, COUNT);
input [7:0] PTR1, PTR2;
input [15:0] ADDRESS, B;
input CONTROL;          // CONTROL is late arriving
output [15:0] COUNT;
parameter [7:0] BASE = 8'b10000000;
wire [7:0] PTR, OFFSET;
wire [15:0] ADDR;
assign PTR = (CONTROL == 1'b1) ? PTR1 : PTR2;
assign OFFSET = BASE - PTR; //Could be any function f(BASE, PTR)
assign ADDR = ADDRESS - {8'h00, OFFSET};
assign COUNT = ADDR + B;
endmodule
```


Duplicated

```
module PRECOMPUTED (ADDRESS, PTR1, PTR2, B, CONTROL, COUNT);
input [7:0] PTR1, PTR2;
input [15:0] ADDRESS, B;
input CONTROL;
output [15:0] COUNT;
parameter [7:0] BASE = 8'b10000000;
wire [7:0] OFFSET1, OFFSET2;
wire [15:0] ADDR1, ADDR2, COUNT1, COUNT2;
assign OFFSET1 = BASE - PTR1; // Could be f(BASE, PTR)
assign OFFSET2 = BASE - PTR2; // Could be f(BASE, PTR)
assign ADDR1 = ADDRESS - {8'h00, OFFSET1};
assign ADDR2 = ADDRESS - {8'h00, OFFSET2};
assign COUNT1 = ADDR1 + B;
assign COUNT2 = ADDR2 + B;
assign COUNT = (CONTROL == 1'b1) ? COUNT1 : COUNT2;
endmodule
```



Coding Skill - Data-path Duplication

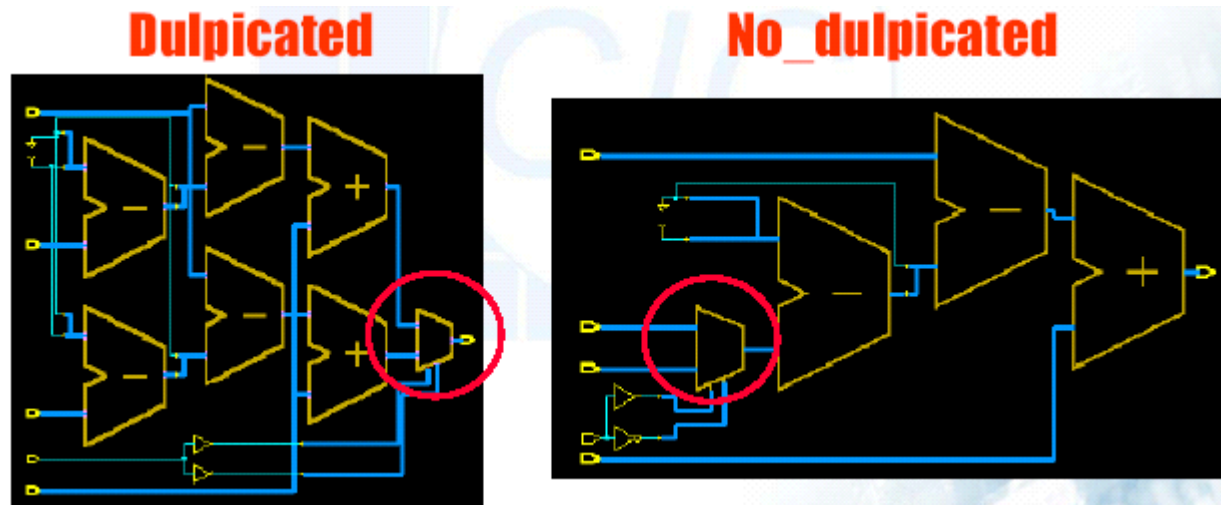- ❖ We assume that signal “**CONTROL**” is the latest arrival pin.
- ❖ By this skill, we will reduce latency but we must pay for it, area!





Coding Skill -- operator in if

- ❖ We assume that signal “A” is latest arrival signal

Before_improved

```
module cond_oper(A, B, C, D, Z);
parameter N = 8;
input [N-1:0] A, B, C, D;
//A is late arriving
output [N-1:0] Z;
reg [N-1:0] Z;

always @(A or B or C or D) begin
if (A + B < 24)
    Z <= C;
else
    Z <= D;
end
endmodule
```

Improved

```
module cond_oper_improved (A, B, C, D, Z);
parameter N = 8;
input [N-1:0] A, B, C, D;
// A is late arriving
output [N-1:0] Z;
reg [N-1:0] Z;

always @(A or B or C or D) begin
if (A < 24 - B)
    Z <= C;
else
    Z <= D;
end
endmodule
```



Coding Skill -- operator in if

- ❖ In this example, not only latency reduced, but also area reduced.

