



100-1 Under-Graduate Project: RTL Coding Style

Speaker: 蘇冠羽

Date: 2011/12/06



Outline

❖ Principles of RTL Coding Styles

- ❖ Readability
- ❖ Finite state machine (FSM)
- ❖ Coding for synthesis
- ❖ Partitioning for synthesis

❖ Debugging Tool: nLint




Pre-RTL Preparation Checklist

- ❖ Communicate design issues with your teammates
 - ❖ Naming conventions, directory trees and other design organizations
- ❖ Have a specification for your design
 - ❖ Everyone should have a specification **BEFORE** they start coding
- ❖ Design partition
 - ❖ Follow the specification's recommendations for partition
 - ❖ Break the design into major functional blocks



RTL Coding Style

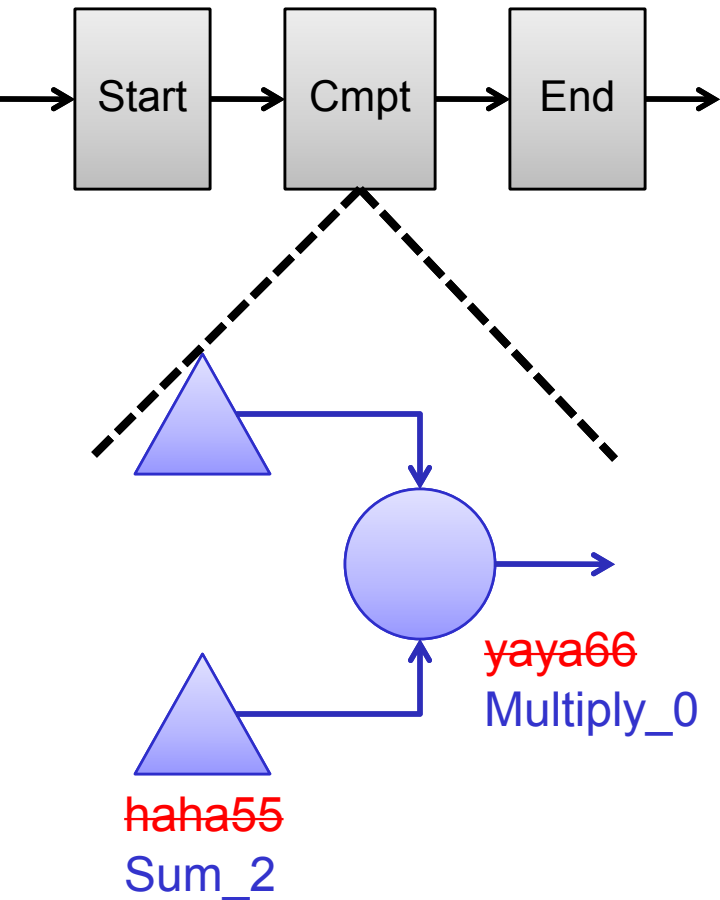

- ❖ Create a block level drawing of your design before you begin coding.
 - ❖ Draw a block diagram of the functions and sub-functions of your design.
- ❖ Hierarchy design
- ❖ Always think of the poor guy who has to read your RTL code.
 - ❖ Easy to understand.
 - ❖ Meaningful names.
 - ❖ Comments and headers.



Outline

❖ Principles of RTL Coding Styles

- ❖ Readability
- ❖ Finite state machine (FSM)
- ❖ Coding for synthesis
- ❖ Partitioning for synthesis

❖ Debugging Tool: nLint



File Headers

- ❖ Include informational header at the top of every source file, including scripts.
 - ❖ Filename
 - ❖ Author information, e.g. name, email...
 - ❖ Description of function and list of key features of the module
 - ❖ Available parameters
 - ❖ Reset scheme and clock domain
 - ❖ Date the file was created and modified
 - ❖ Critical timing and asynchronous interface



File Header Example: DCT.v

```

1 // =====
2 // COPYRIGHT (c) 2007 Chin-Yu Chen. ALL RIGHTS RESERVED
3 // -----
4 // FILE NAME      : dct.v
5 // TYPE           : top module
6 // DEPARTMENT      : Access Lab, Graduate Institute of Electronics Engineering, National Taiwan University
7 // AUTHOR          : Chin-Yu Chen
8 // AUTHOR'S EMAIL : doow@access.ee.ntu.edu.tw
9 // PURPOSE         : A real-time discrete cosine transform(DCT) implemetation
10 // -----
11 // =====
12 // REVISION HISTORY
13 //
14 //      DATE          VERSION      AUTHOR          COMMENTS
15 //      -----
16 //      2007/05/30   1.0           Chin-Yu Chen   First creation
17 // =====
18 // PARAMETERS
19 //
20 //      PARA_NAME     RANGE        COMMENTS        DEFAULT
21 //      -----
22 //      DATA_WIDTH   [8,16]       Width of data   8
23 // =====
24 // REUSE ISSUES
25 //
26 // RESET STRATEGY    : asynchronous reset
27 // CLOCK DOMAINS     : posedge trigger clock
28 // =====

```



Identifiers Naming Rule

- ❖ Begin with an alpha character (a-z, A-Z) or an underscore (_) and can contain alphanumeric, dollar signs (\$) and underscore.
 - ❖ Examples of illegal identifiers:
 - 34net
 - a*b_net
 - n@238
- ❖ Up to 1023 characters long
- ❖ **Case sensitive**
 - ❖ e.g. sel and SEL are different identifiers



General Naming Conventions(1/3)

- ❖ **Lowercase letters** for all signals, variables, and port names.
 - ❖ reg is used in procedural block
- ❖ **Uppercase letters** for constants and user-defined types.
 - ❖ e.g. ``define MEM_WIDTH 16`
- ❖ Verilog is **case sensitive**
- ❖ Meaningful names
 - ❖ Use *ram_addr* for RAM address bus instead of *ra*



General Naming Conventions(2/3)


- ❖ Use *clk* for the clock signal
 - ❖ If more than one clock, use *clk* as the prefix for all clock signals (*clk1*, *clk2*, *clk_interface*)

- ❖ For active low signals, use **_n*
 - ❖ If the reset signal is active low, use *rst_n*
 - ❖ Similarly, for active high signals, use **_p*

- ❖ For input of a register, use **_w*
- ❖ For output of a register, use **_r*
- ❖ For input signals, use **_i*
- ❖ For output signals, use **_o*



Example

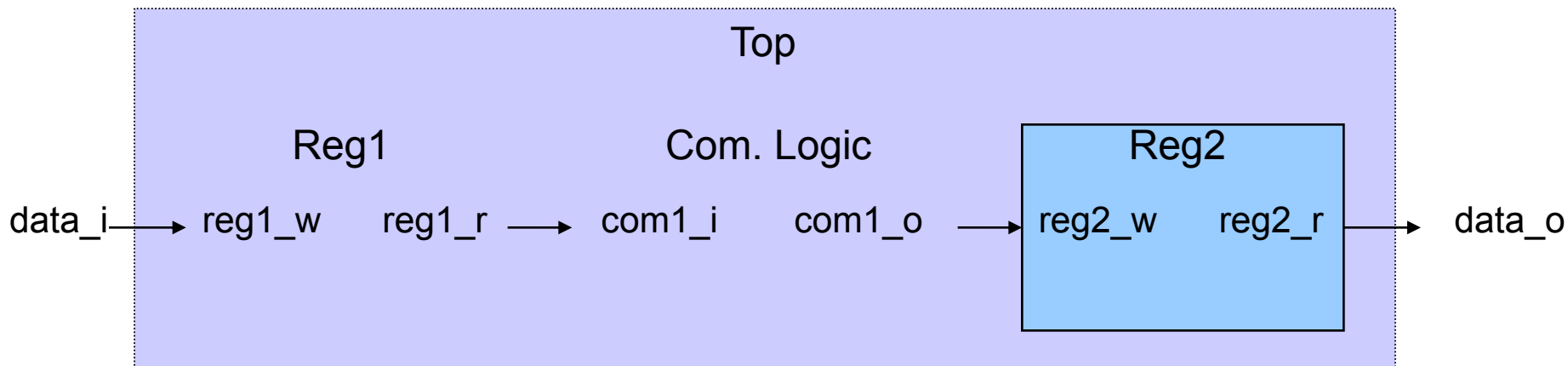

```
assign reg1_w = data_i;
assign reg2_w = com1_o;
assign com1_i = reg1_r;
```

```
always @ (posedge clk_p) begin
    reg1_r <= reg1_w;
    reg2_r <= reg2_w;
end
```

```
always @(*) begin
    com1_o = com1_i + 4'd5;
end
```

For connection

Logic



General Naming Conventions(3/3)

- ❖ Use $[x:0]$ (instead of $[0:x]$) when describing multi-bit buses

- ❖ A somewhat arbitrary suggested “standard”

- ❖ Use parameter to improve readability

- ❖ module car (out, in1, in2);

.....

parameter S0_STOP = 2'd0, S1_RUN = 2'd1;

.....

case (state) S0_STOP:

.....

- ❖ Don't use HDL reserved words

- ❖ e.g. xor, nand , module



Use comments

- ❖ Use comments appropriately to explain
 - ❖ Brief, concise, explanatory
 - ❖ Avoid “comment clutter”— obvious functionality does not need to be commented
- ❖ Single-line comments begin with //
- ❖ Multiple-line comments start with /* and end with */
- ❖ Use indentation to improve the readability of continued code lines and nested loops

❖ e.g.

```
if(a)
    if(b)
        if(c)
```



Module Instantiation

- ❖ Always use explicit mapping for ports, use **named mapping** rather than positional mapping

```
DW_ram_r_w_s_dff
#((`ram_data_width+`ram_be_data_width),
  (`fifo_depth),1)
U_int_txf_ram (
  .clk          (refclk),
  .rst_n        (txfifo_ram_reset_n),
  .cs_n         (1'b0),
  .wr_n         (txfifo_wr_en_n),
  .rd_addr      (txfifo_rd_addr),
  .wr_addr      (txfifo_wr_addr),
  .data_in      (txfifo_wr_data),
  .data_out     (txf_ram_data_out)
);
```



```
module_a (
  clk,
  s1_i,
  s1_o,
  s2_i,
  s2_o
);
```





Use loops and arrays

❖ Using loop to increase readability

- ❖ Loop is usually used as memory initialization
for example:

```
module my_module( ... );  
  
...  
reg [31:0] reg_file[15:0];  
integer tmp;  
  
always @(posedge clk or posedge rst)  
if(rst)  
for(tmp=0; tmp<16; tmp++)  
    reg_file[tmp] <= 32'd0;  
  
...
```



Outline

❖ Principles of RTL Coding Styles

- ❖ Readability
- ❖ Finite state machine (FSM)
- ❖ Coding for synthesis
- ❖ Partitioning for synthesis


❖ Debugging Tool: nLint




Finite State Machines

- ❖ FSM have widespread application in digital systems.
 - ❖ Most frequently used in controller
- ❖ Mealy Machine: The next state and **the outputs** depend on the present state and the inputs.
- ❖ Moore Machine: The next state depends on the present state and the inputs, **but the output** depends on only the present state.

Mealy machine

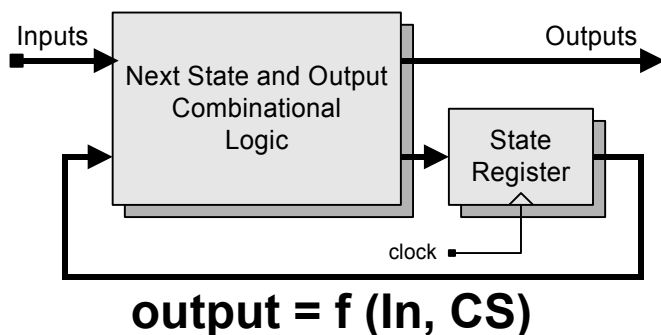

Moore machine

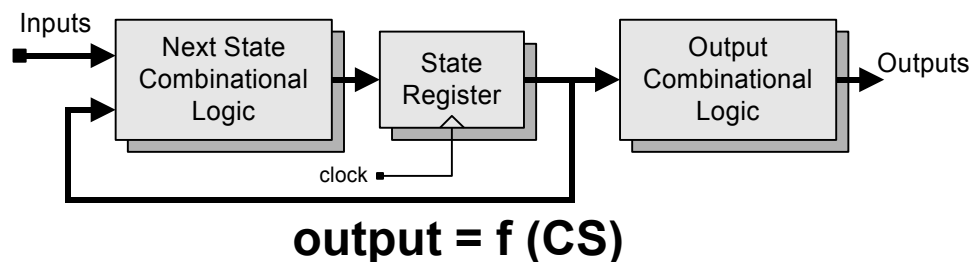



Modeling FSM in Verilog

❖ Sequential Circuits

- ❖ Memory elements of States (S)

❖ Combinational Circuits

- ❖ Next-state Logic (NL)
- ❖ Output Logic (OL)

❖ Three coding styles

- ❖ (1) Separate S, OL and NL
- ❖ (2) Combines NL+ OL, separate S
- ❖ (3) Combine S + NL, separate OL ☐ **Not recommended!!**

Mix the comb. and seq. circuits



Style (1) Separate S, NL, OL

- S

```
always @ (posedge clk)
    current_state <= next_state;
```

- NL

```
always @ (current_state or In)
    case (current_state)
        S0: case (In)
            In0: next_state = S1;
            In1: next_state = S0;
            . . .
        endcase //In
        S1: . . .
        S2: . . .
    endcase //current_state
```

- OL

```
// if Moore
always @ (current_state)
    case(current_state)
        S0: z = output_value;
```

```
// if Mealy
always @ (current_state or In)
    case(current_state)
        S0: if(In==0) z = output_value;
            else ...
```



Style (2) Combine NL+OL; Separate S

- S

```
always @ (posedge clk)
    current_state <= next_state;
```

- NL+OL

```
always @ (current_state or In)
    case (current_state)
        S0: begin
            case (In)
                In0: begin
                    next_state<= S1;
                    Z =values; // Mealy
                end
                In1: . . .
            endcase // In
            Z =values; // Moore
        end //S0
        S1: . . .
    endcase // current_state
```



Outline

❖ Principles of RTL Coding Styles

- ❖ Readability
- ❖ Finite state machine (FSM)
- ❖ Coding for synthesis
- ❖ Partitioning for synthesis

❖ Debugging Tool: nLint



Reset Signal

- ❖ Use the reset signal to initialize registered signals

```
// process with asynchronous reset
always @(posedge clk or posedge rst_a)
begin : ex5-20_proc
    if (rst_a == 1'b1)
        begin
            ...    dct_r <= 1'b0;
        end
    else begin
        ...    dct_r <= dct_w;
    end
end // ex5-20_proc
```



Avoid Latches (1/2)

- ❖ Avoid using any latches in your design
- ❖ Use a design checking tool (nLint) to check for latches in your design

- ❖ Poor Coding Styles

- ❖ Latch inferred because of missing else condition

```
always @(a or b)
begin
    if (a == 1'b1)
        q <= b;
    end
```

- ❖ Latches inferred because of missing assignments and missing condition

```
always @(d)
begin
    case (d)
        2'b00: z <= 1'b1;
        2'b01: z <= 1'b0;
        2'b10: z <= 1'b1; s <= 1'b1;
    endcase
end
```



Avoid Latches (2/2)

❖ Avoid inferred latches

- ❖ Fully assign outputs for all input conditions

Poor coding style:

```
always @(g or a or b)
begin
    if (g == 1'b1)
        q <= 0;
    else if (a == 1'b1)
        q <= b;
end
```


Recommended coding style:

```
always @(g1 or g2 or a or b)
begin
    q <= 1'b0 ;
    if (g1 == 1'b1)
        q <= a;
    else if (g2 == 1'b1)
        q <= b;
end
```





Avoid Combinational Feedback

Bad: Combinational processes are looped

 

 Good: Combinational processes are not looped





Sensitivity List (1/3)

- ❖ For combinational blocks, the sensitivity list must include every signal that is read by the process.
 - ❖ Signals that appear on the right side of an assign statement
 - ❖ Signals that appear in a conditional expression

```
always @(a or inc_dec)
begin : COMBINATIONAL_PROC
    if (inc_dec == 0)
        sum = a + 1;
    else
        sum = a - 1;
end // COMBINATIONAL_PROC
```

- ❖ For simplicity, Verilog 2001 supports *always @ (*)*




Sensitivity List (2/3)

- ❖ Include a complete sensitivity list in each of *always* blocks
 - ❖ If not, the behavior of the pre-synthesis design may differ from that of the post-synthesis netlist.

Incomplete sensitivity list

```
always @ (a)  
c <= a or b;
```


Pre-synthesis
Simulation
Waveform

 

Synthesized
Netlist



Post-synthesis
Simulation
Waveform

 



Sensitivity List (3/3)

❖ For sequential blocks

- ❖ The sensitive list must include the clock signal.
- ❖ If an asynchronous reset signal is used, include reset in the sensitivity list.

```
always @(posedge clk)
begin : SEQUENTIAL_PROC
    q <= d;
end // SEQUENTIAL_PROC
```

❖ Use only necessary signals in the sensitivity lists


- ❖ Unnecessary signals in the sensitivity list slow down simulation



Combinational vs. Sequential Blocks


❖ Combinational logic

 - ❖ Use **blocking (=)** assignments
- ❖ Execute in sequential order




❖ Sequential logic

 - ❖ Use **nonblocking (<=)** assignments
- ❖ Execute concurrently



- ❖ Do not make assignments to the same variable from more than one *always* block.


Multiple Assignment

 



case Statement

 - ❖ Fully specified verilog *case* statements result in a single-level multiplexer
- ❖ Partially specified Verilog *case* statements result in latches




```
case (sel)
  2'b00: outc = a;
  2'b01: outc = b;
  2'b10: outc = c;
  default: outc = d;
endcase;
```



if-then-else Statement

 - ❖ An *if-then-else* statement infers a priority-encoded, cascaded combination of multiplexers.



```
if (sel == 2'b00)
    outi = a;
else if (sel == 2'b01)
    outi = b;
else if (sel == 2'b10)
    outi = c;
else
    outi = d;
```



case vs. *if-then-else* Statements

- ❖ *case* statements are preferred if the priority-encoding structure is not required
 - ❖ The multiplexer is faster.
- ❖ *if-then-else* statement can be useful if you have a late-arriving signal
 - ❖ Connect the signal to *a* in last slide
- ❖ A conditional assignment may also be used to infer a multiplexer.

assign *z* = (*sel_a*) ? *a* : *b*;



Outline

❖ Principles of RTL Coding Styles

- ❖ Readability
- ❖ Finite state machine (FSM)
- ❖ Coding for synthesis
- ❖ Partitioning for synthesis

❖ Debugging Tool: nLint



Register All Outputs

- ❖ For each subblock of a hierarchical macro design, **register all output signals** from the subblock.
 - ❖ Makes output drive strengths and input delays predictable


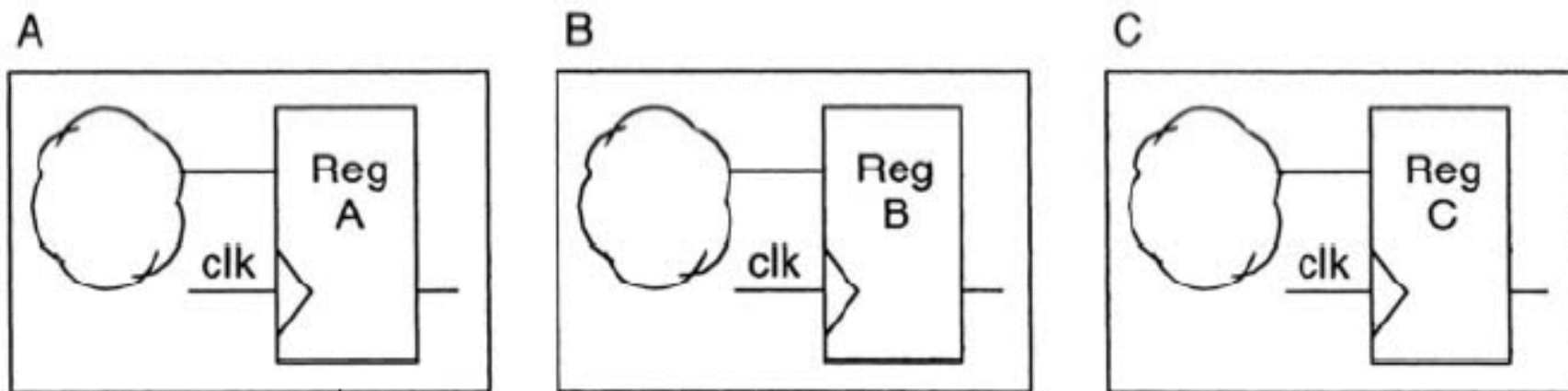


Figure Good example: All output signals are registered

 


Related Combinational Logic in a Single Module


- ❖ Keep related combinational logic together in the same module



Bad

 

Better

 

Best



Outline

❖ Principles of RTL Coding Styles


- ❖ Readability
- ❖ Finite state machine (FSM)
- ❖ Coding for synthesis
- ❖ Partitioning for synthesis

❖ Debugging Tool: nLint




GUI

❖ nLint -gui &

 




Import Design

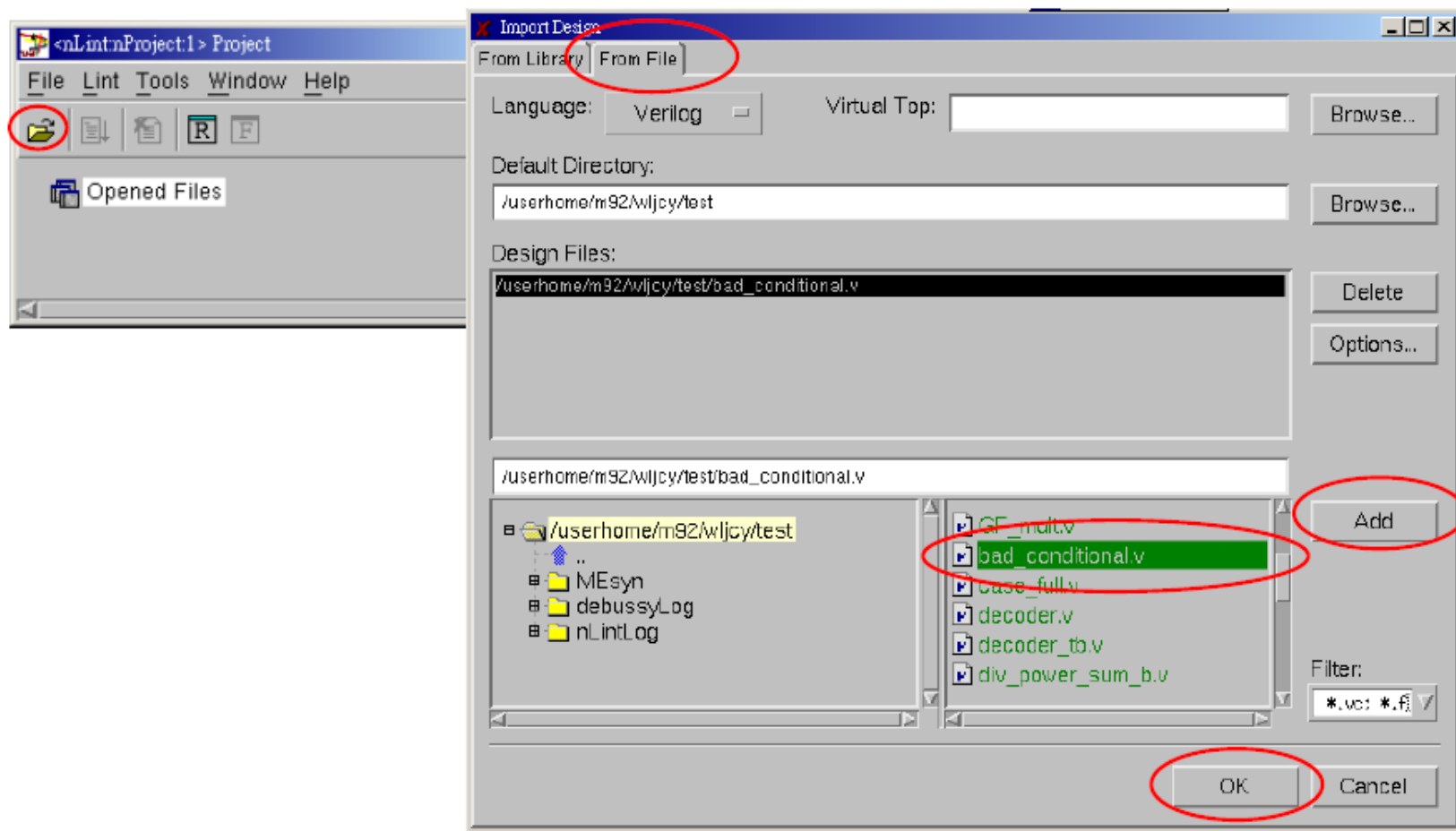





Edit File

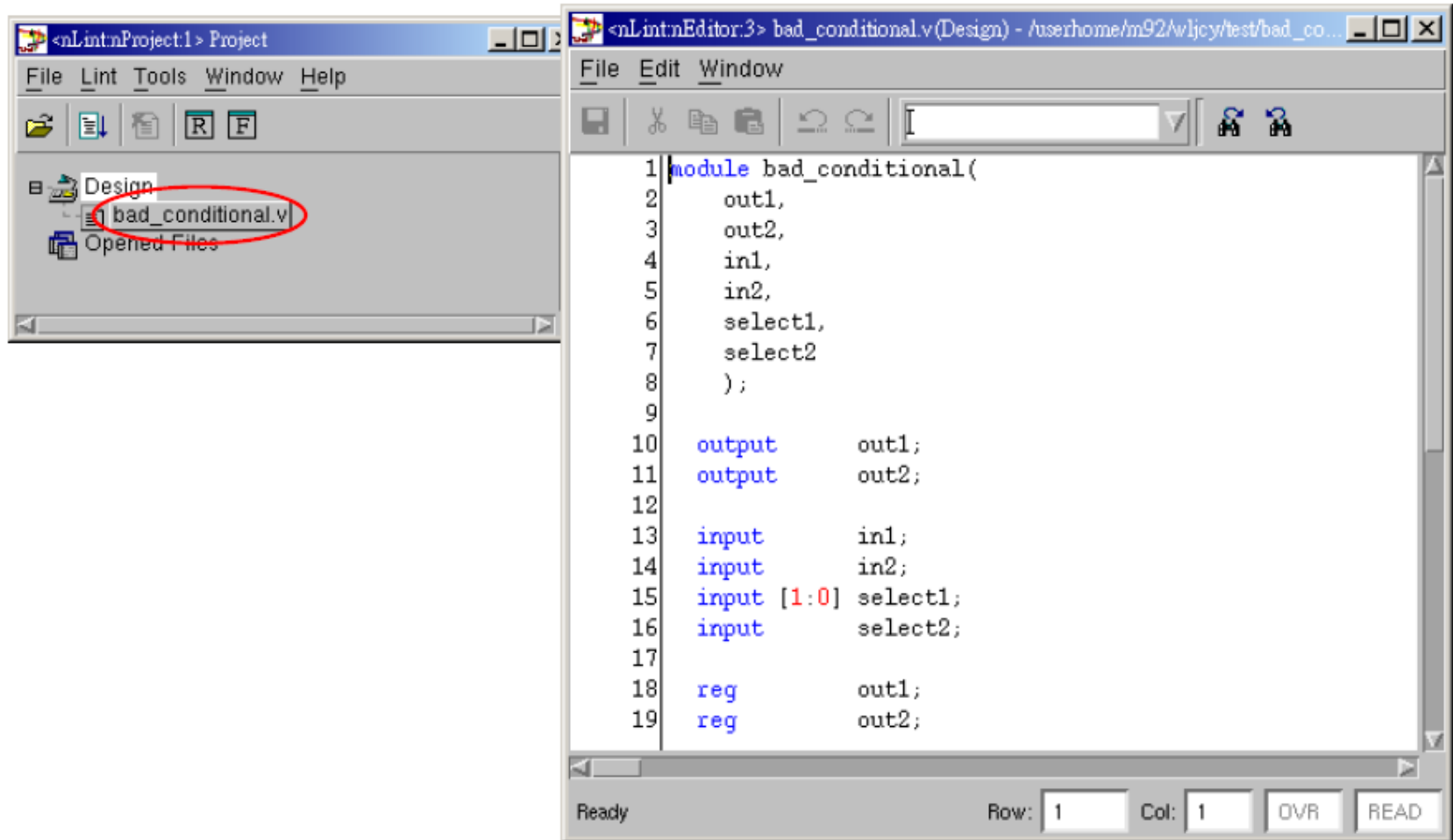




Lint -> Run

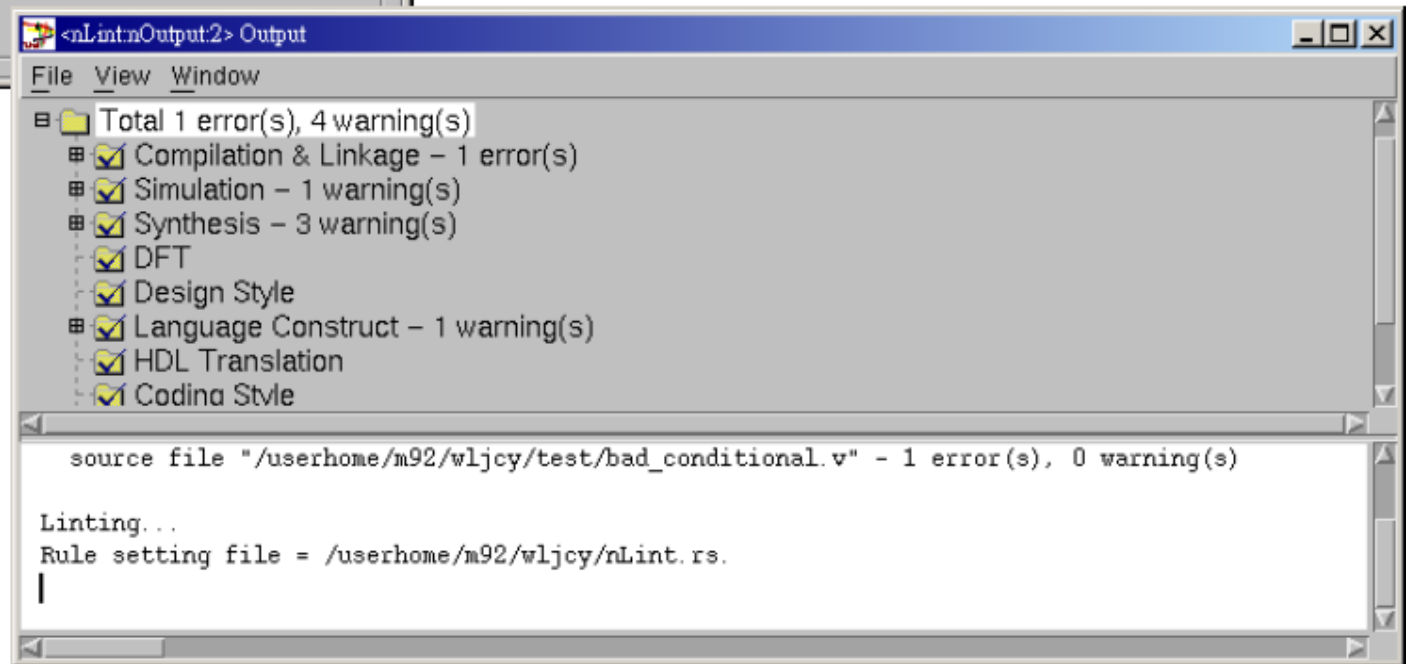 



Fix Warning 1

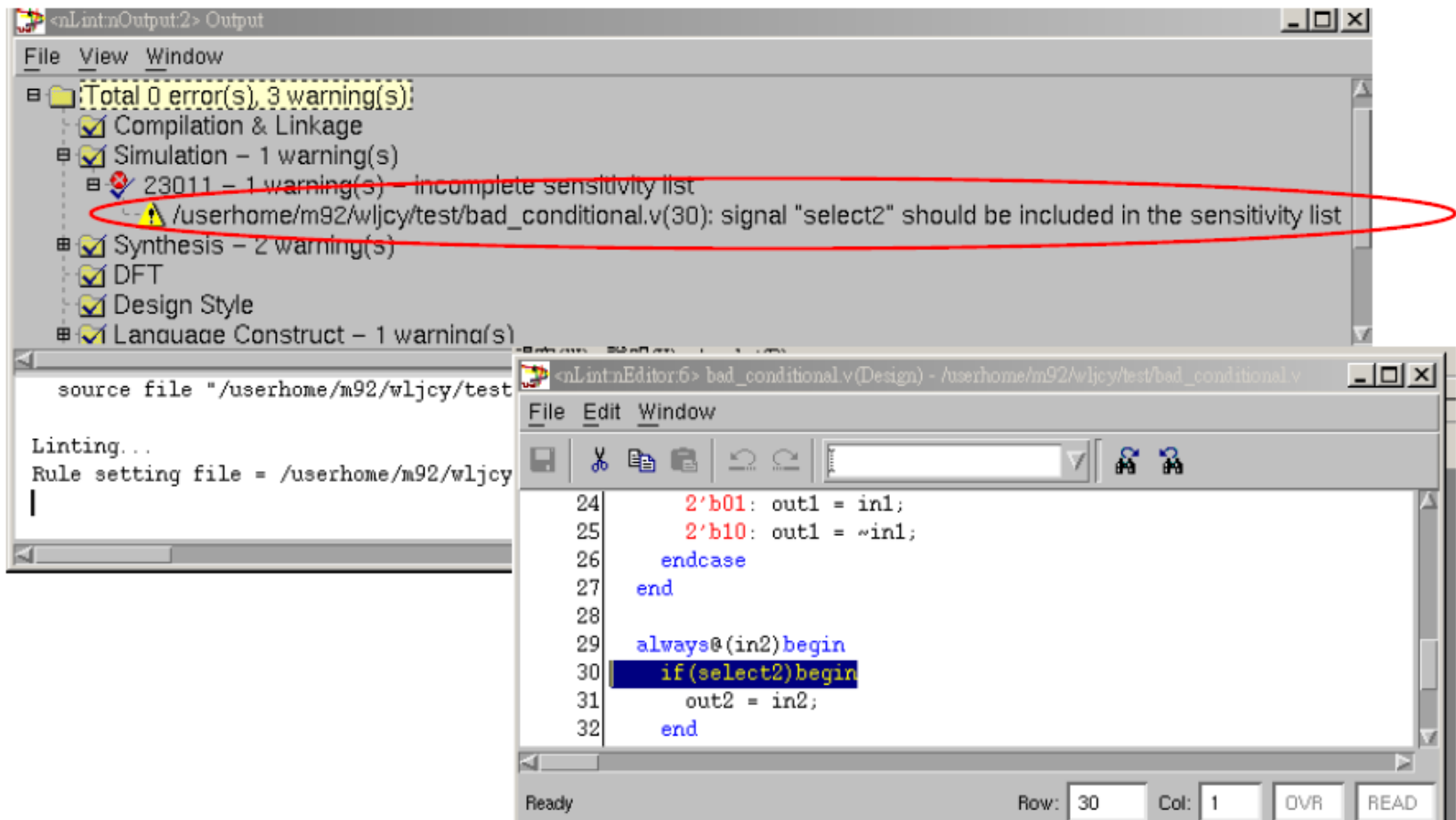



Search Rule

❖ Right click -> Search Rule

The screenshot shows a software interface with a project tree on the left and a message window on the right. The project tree lists various stages: Total 0 error(s), 2 warning(s); Compilation & Linkage; Simulation; Synthesis - 1 warning(s); 23003 - 1 warning(s) - Inferred latch; /userhome/m92/wljcy/test/bad_conditional.v(23): latch inferred on signal "out1"; DFT; Design Style; and Language Construct - 1 warning(s). The message window displays the following information:

source file "/userhome/m92/wljcy/test/bad_conditional.v(23): latch inferred on signal "out1"

Linting...
Rule setting file = /userhome/m92/wljcy/r

23003 inferred latch

Message


%f(%l): Warning %n: latch inferred on signal %s

Configurable Parameter

Rule group: Synthesis;
Argument type: none;



No Error & Warning

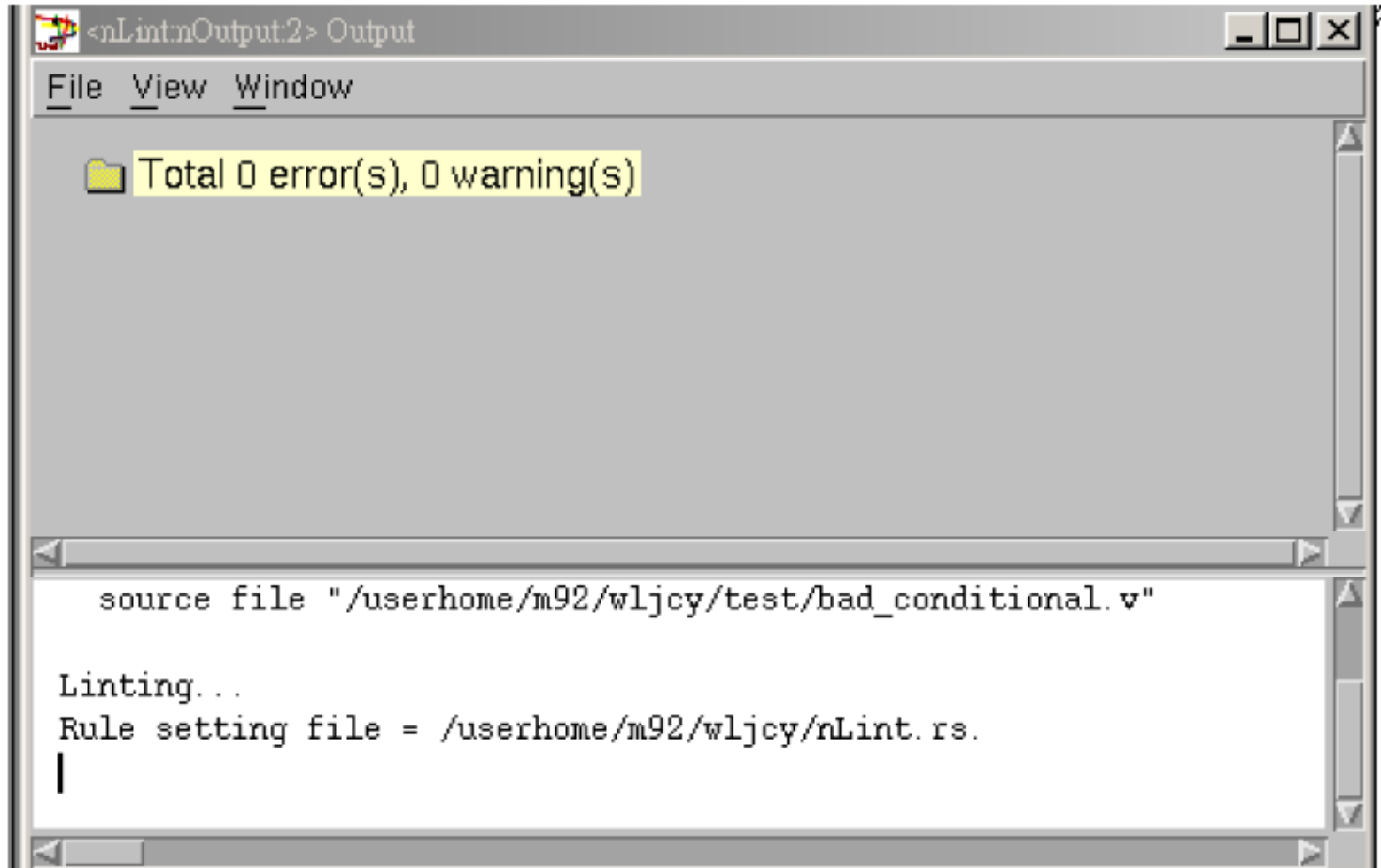



Check for Synthesizable (1/2)

❖ *SpringSoft nLint*

- ❖ Check for correct mapping of your design
- ❖ Not so power in detecting latches

❖ *Synopsys Design Compiler*

- ❖ Synthesis Tool
- ❖ The embedded *Presto Compiler* can list your flip-flops and latches in details
 - > `dv -no_gui`
 - > `read_verilog yourdesign.v`



Check for Synthesizable (2/2)

```
Inferred memory devices in process
in routine cache line 281 in file
'/home/m97/gieks/cache/cache.v'.
```

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
block6_reg	Flip-flop	155	Y	N	Y	N	N	N	N
block7_reg	Flip-flop	155	Y	N	Y	N	N	N	N
block0_reg	Flip-flop	155	Y	N	Y	N	N	N	N
state_reg	Flip-flop	2	Y	N	Y	N	N	N	N
block1_reg	Flip-flop	155	Y	N	Y	N	N	N	N
mem_fetching_reg	Flip-flop	1	N	N	Y	N	N	N	N
block3_reg	Flip-flop	155	Y	N	Y	N	N	N	N
block5_reg	Flip-flop	155	Y	N	Y	N	N	N	N
block2_reg	Flip-flop	155	Y	N	Y	N	N	N	N
block4_reg	Flip-flop	155	Y	N	Y	N	N	N	N

```
Presto compilation completed successfully.
```

```
Current design is now '/home/m97/gieks/cache/cache.db:cache'
```

```
Loaded 1 design.
```

```
Current design is 'cache'.
```

```
cache
```

```
design_vision>
```

Checking latches
using Design Compiler